

SISTEMAS DIGITALES



ARITHMETIC-LOGIC UNIT

Victor Moreno Arribas

α180070

Jorge Albendea Pizarro

190229

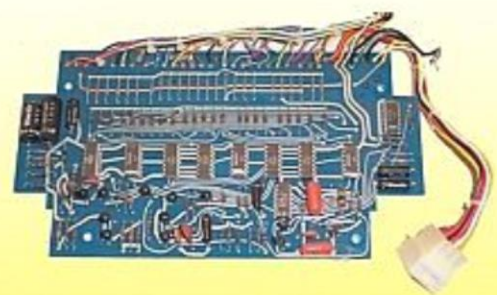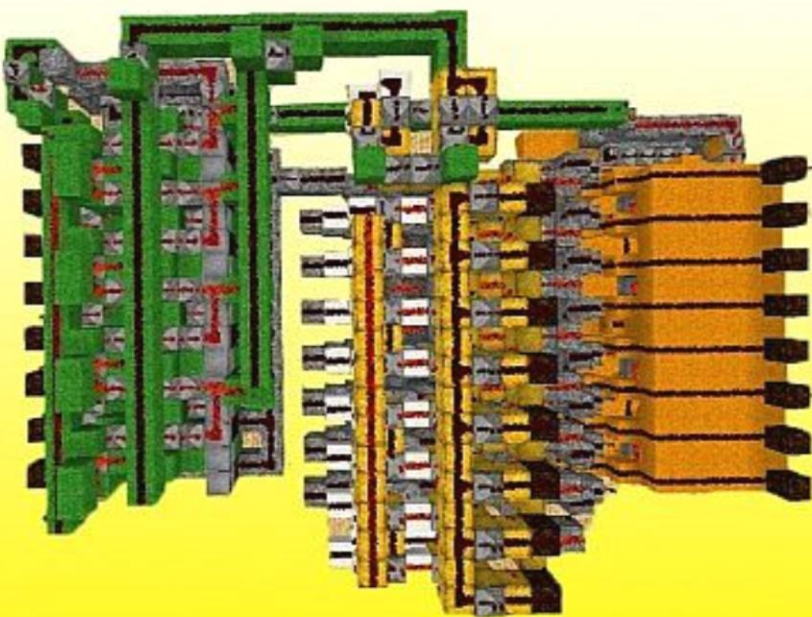

Minecraft
multiplication
ALU module

SUMMARY

Select the slide you want to see.

A

B

C

D

E

F

G

H

I

A

B

C

D

E


F

G

H

I

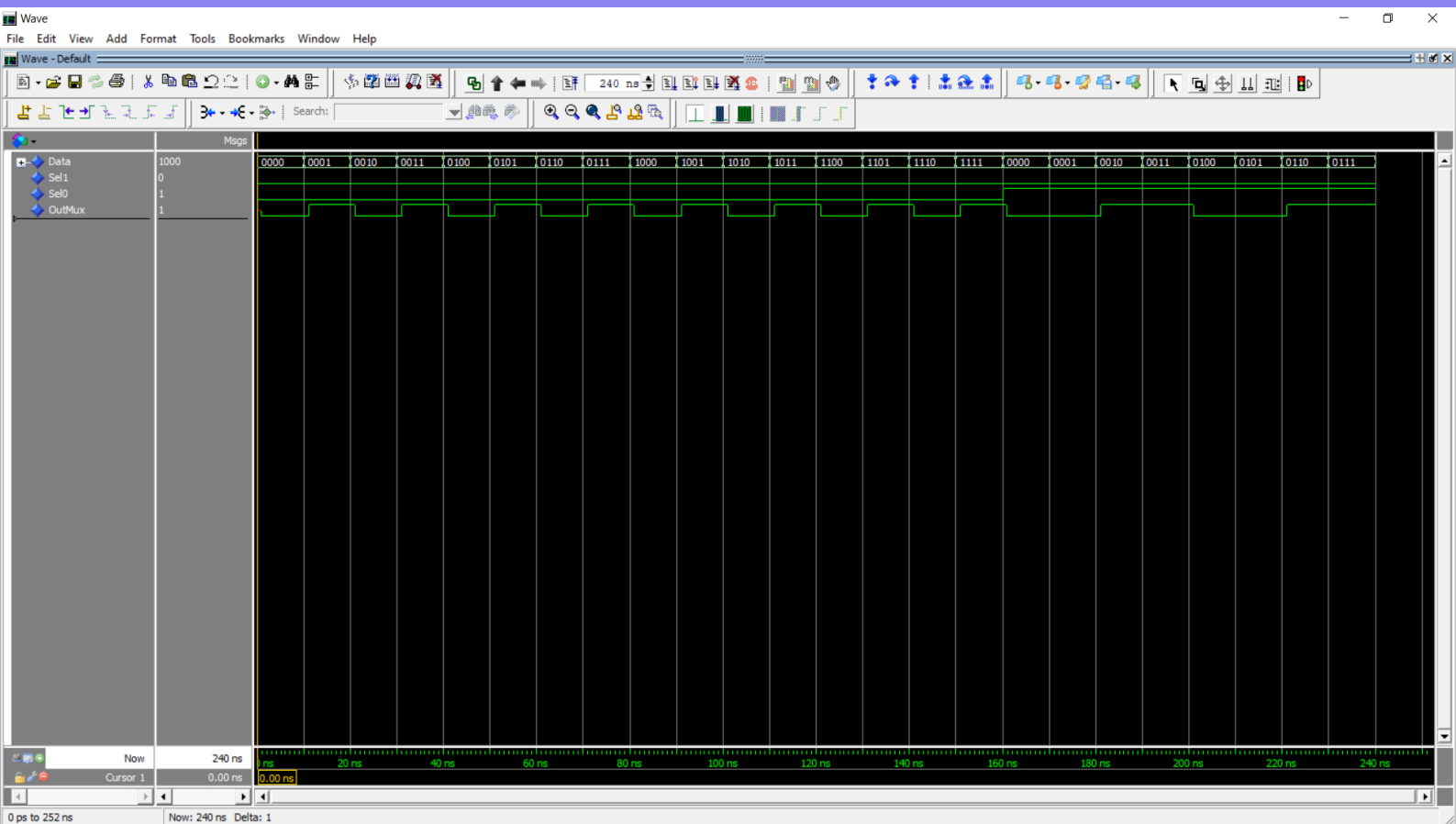Get a screenshot of the whole 640 ns simulation.




Options:

1. You can download the image.

Click para descargar la imagen 

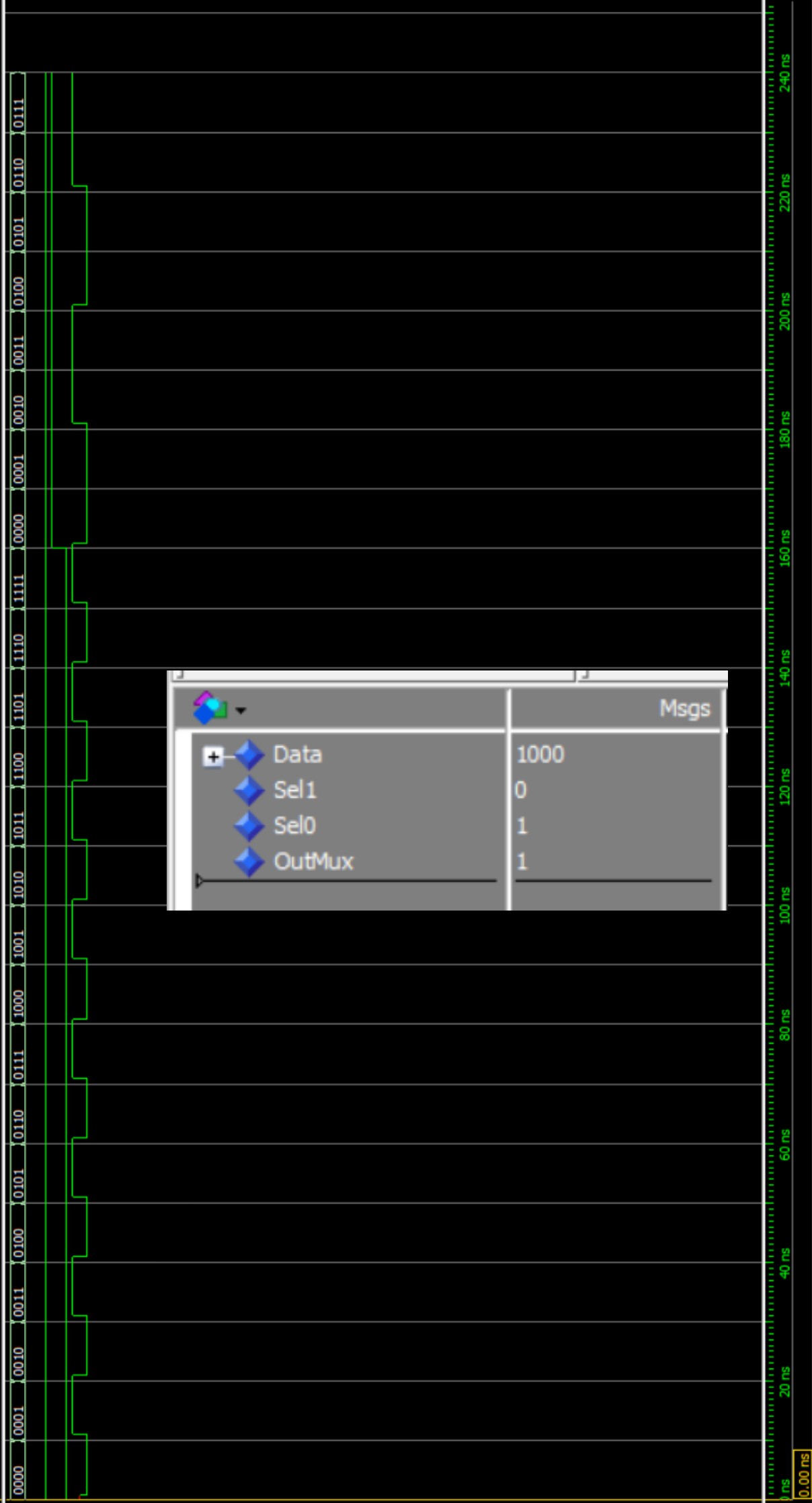2. In the next slide, i tried to make the image as big as posible.



A**B****C****D****E****F****G****H****I**

What would the output be if all of the data inputs are 'Z'?

How well do you think your code reflects the real behavior of a multiplexor built with NAND gates?

In the simulation with the undefined data inputs ('Z') we get a set output because it considers the output to be disconnected.

The code does not reflect the real behavior of a multiplexor because when the data inputs are undefined there would be an undefined output, but this does not mean that there is no output (that is disconnected) it just mean its undefined.

The output of a multiplexor that receives a set of undefined inputs should get an output that has an undefined value.

When we run the simulation we observe that the output didn't get any value during the whole period of simulation, we tried with different times of simulation but in all of them the output wasn't on the screen. So our multiplexor doesn't have a real behavior.

A

B

C

D

E


F

G

H

I

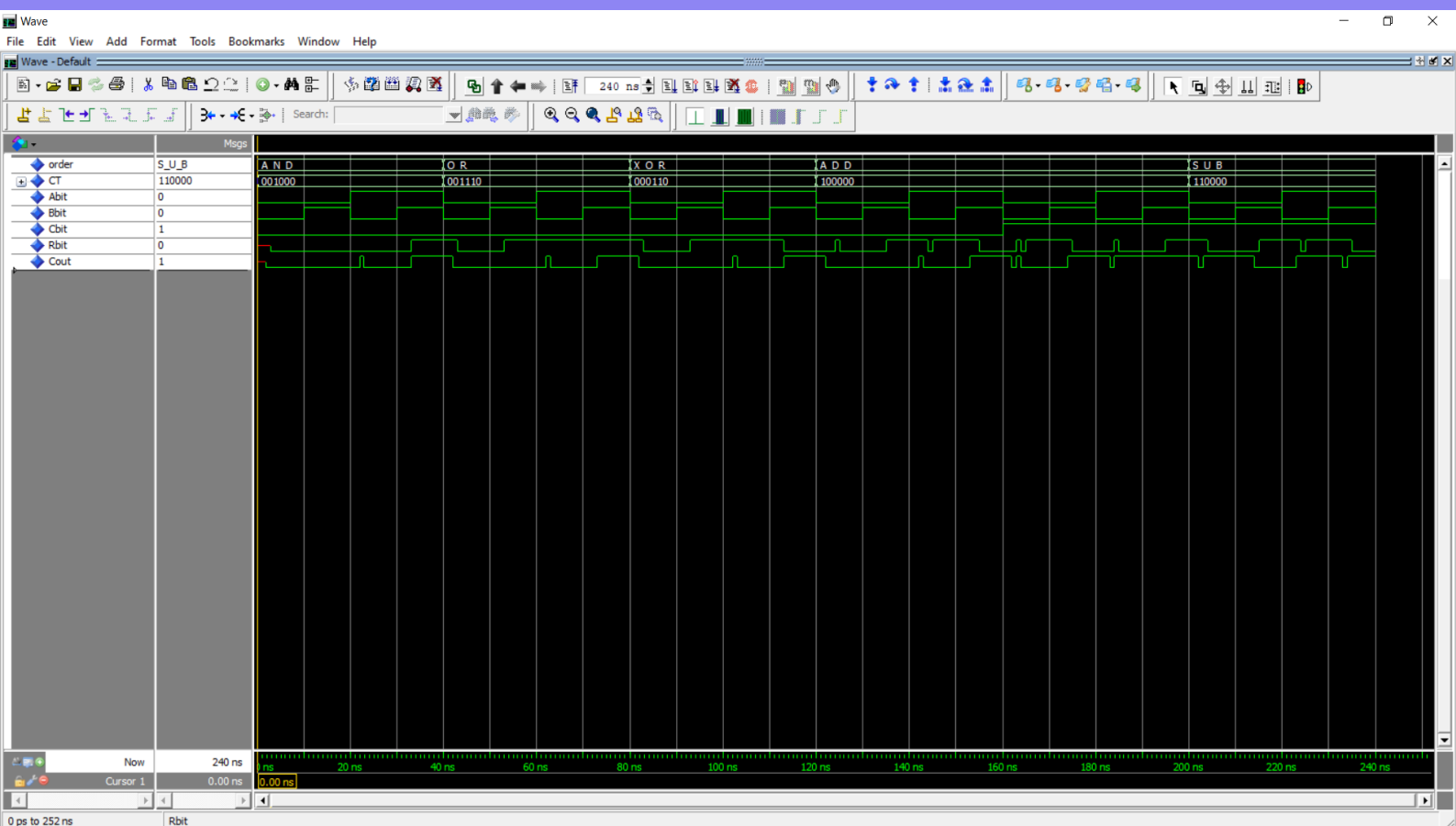Get a screenshot of the whole 240 ns simulation of the bitslice.




Options:

1. You can download the image.

Click para descargar la imagen 

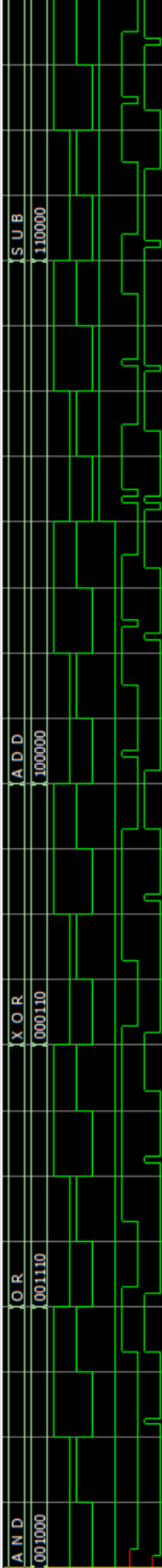2. In the next slide, i tried to make the image as big as posible.



order	S_U_B
CT	110000
Abit	0
Bbit	0
Cbit	1
Rbit	0
Cout	1

A

B

C

D

E

F

G

H

I

Explain which combinations of the control signals (values of the CTi) are needed to perform each of the operations tested and which values would be needed to test the logical NAND function.

We have 6 control signals from 5 down to 0.
We can have $2^6 = 64$ combinations.

In the test the control signals were established for:
AND at 001000, OR at 001110, XOR at 000110, ADD at 100000 and for SUB at 110000.

A

B

C

D

E

F


G

H

I

Get a screenshot showing the behaviour of the circuit when doing an AND logical function, being its inputs $A = a_2a_1a_0 = 101$ and $B = b_2b_1b_0 = 011$.

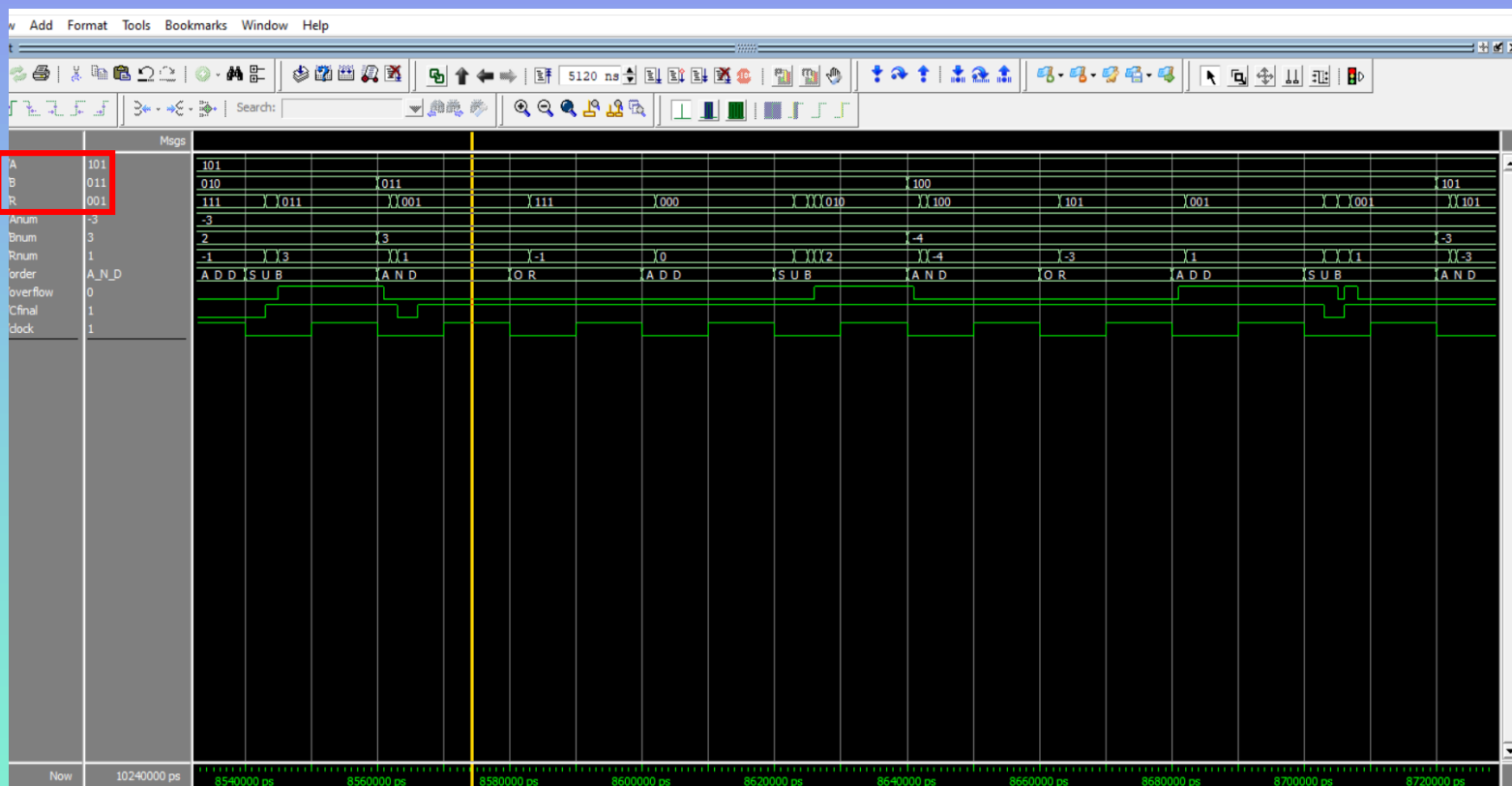Explain the result obtained in R. Make sure that the cursor is placed on a time instant in which these values happen.



The final value of R is 001, when that happens A still has a value of 101 but B has changed to 011.

As we can observe in the image, the R value is obtained at the yellow line which is **857500 ps = 857 ns** but is just one of the possible times, because we could have positioned the yellow line a little bit more to the right.

101																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																				
-----	--	--	--	--	--

A

B

C

D

E

F


G

H

I

Do the same thing (including the position of the cursor) but for the ADD function with $A = 010$ and $B = 100$.

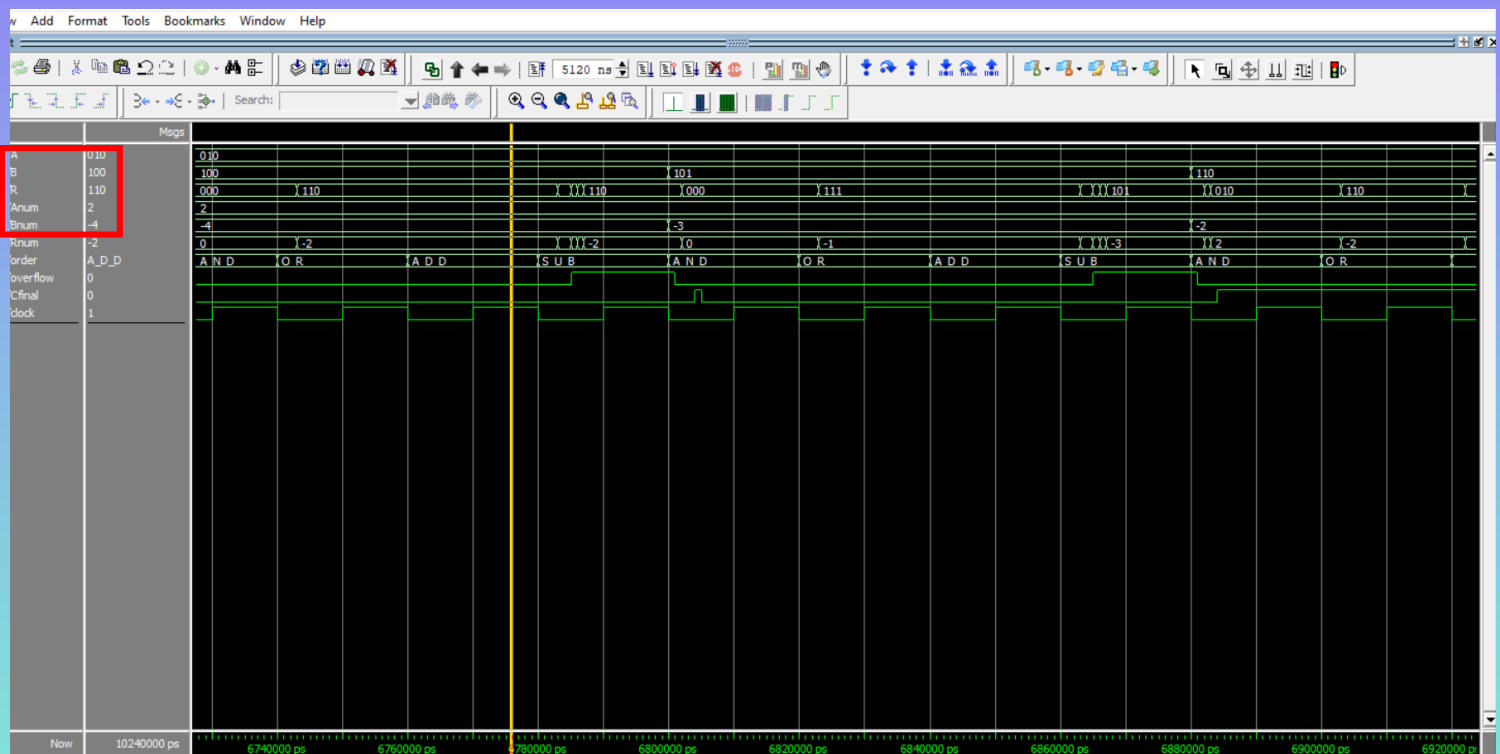Explain the values of the result Rnum, the Overflow and the final carry Cfinal.



Starting with $A=010$ and $B=100$, so translated to decimal $A=2$ and $B=-4$ because is in 2's complements (B starts by 1 so its negative). Then Rnum is -2 because $Anum + Bnum = 2 + (-4) = -2$ which translated to 2's complement is $R=110$ as we can observe.

Doing the sum there is no carry so $Cfinal = 0$ and there is no overflow either.

A

B

C

D

E


F

G

H

I

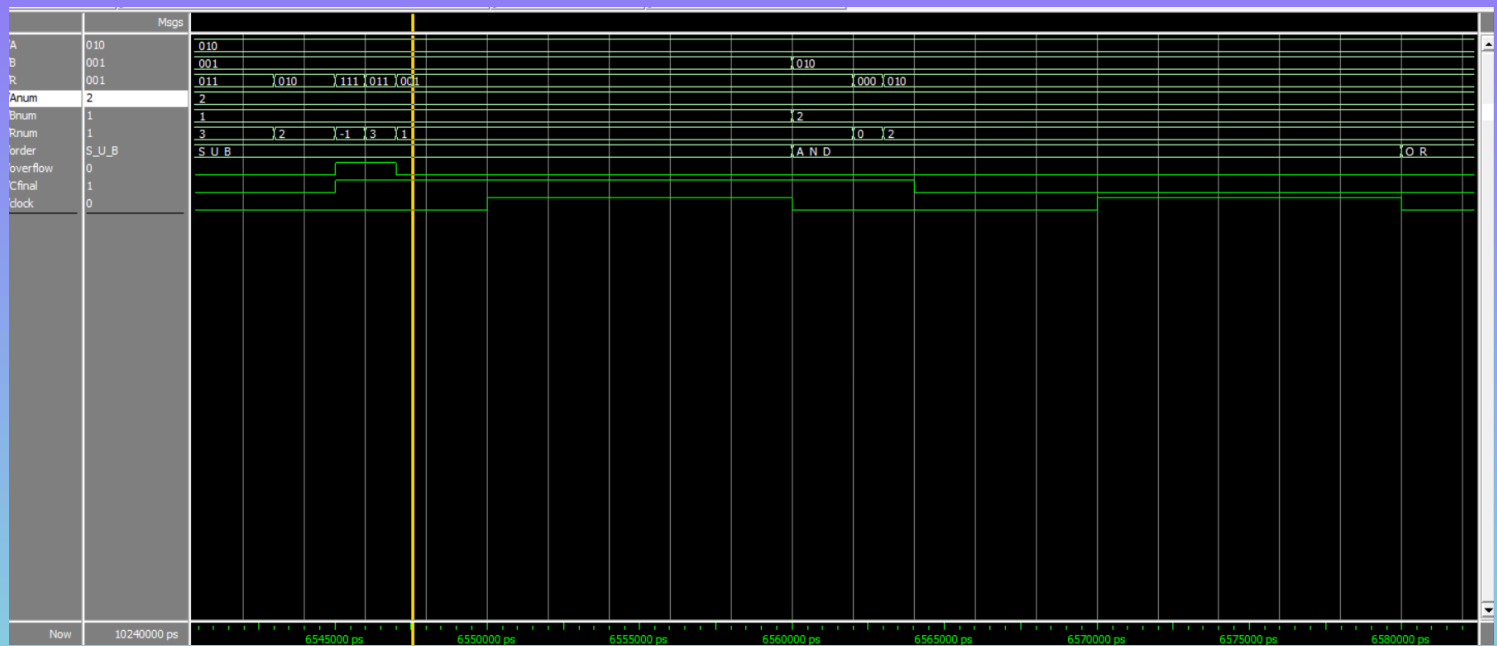Do the exactly the same thing but for the SUBtract function with $A = 010$ and $B = 001$. Explain the values of Rnum, the Overflow and the final carry Cfinal.



Now we have $A=010$ and $B=001$.

Now $Anum = 2$ and $Bnum = 1$.

After the SUB we obtained $R=001$ which equal to $Rnum = 1$.

The Cfinal is active or '1' because in the operation $0 - 1$ at the beginning we obtained a carry value of '1' while the overflow stills on '0' again.

A

B

C

D

E


F

G

H

I

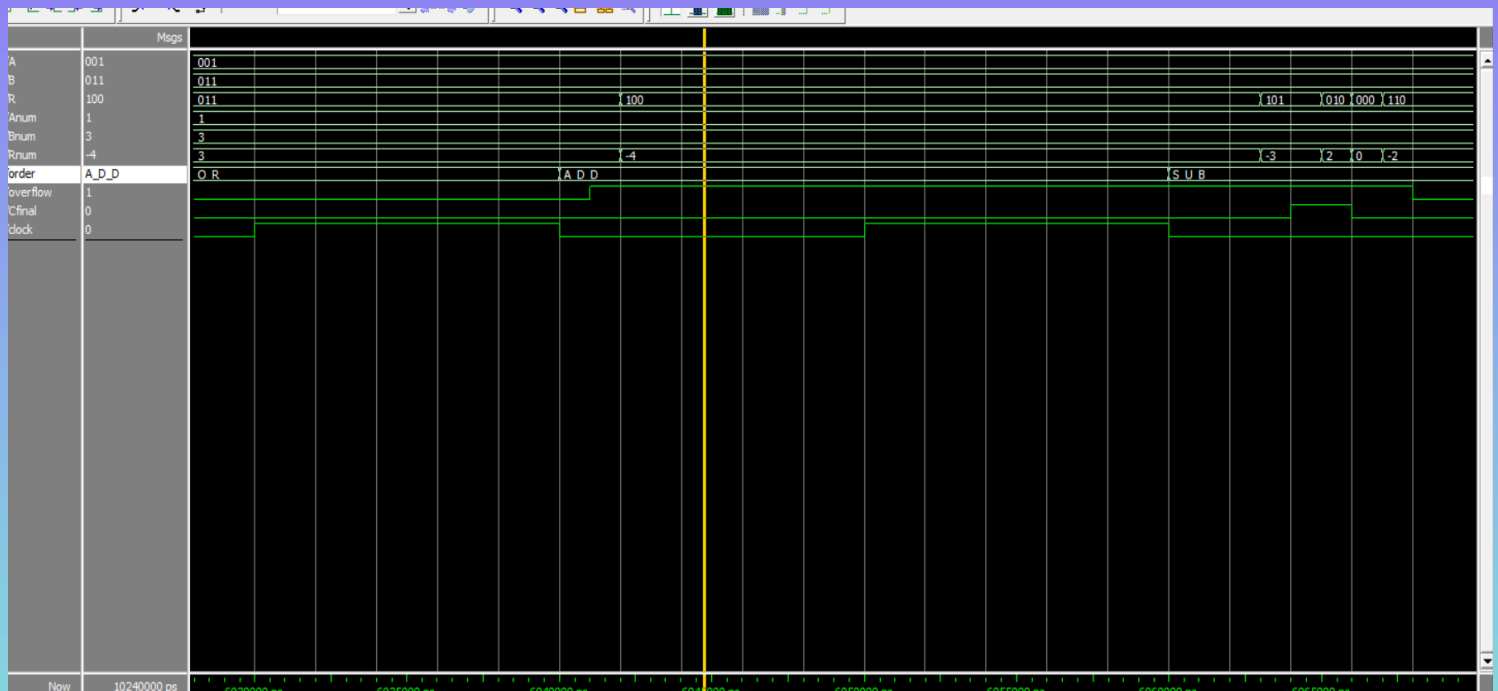Get a screenshot in which the circuit is adding and there is an overflow (place the cursor marking the overflow).
Explain why such overflow is generated.



As we can there is an overflow because the overflow signal is activated. That overflow is given because the result of the sum of $001 + 011$ is over the range of representation.

A

B

C

D

E

F

G

H

I

Get a screenshot in which the circuit is subtracting and there is an overflow (place the cursor marking the overflow). Explain why such overflow is generated.



Now we started with A=001 and 001 which translates to Anum=1 and Bnum=1. The overflow signal only has sense when we are treating signed data, so in this case the overflow is activated once the Rnum should obtain the -5 value, but that can't be represented with one sign bit and two value bits.



POLITÉCNICA

“Ingeniamos el futuro”

**CAMPUS
DE EXCELENCIA
INTERNACIONAL**



**E.T.S. de Ingenieros
Informaticos**



***dat**si*

