

Third Project


16-bit CPU

Victor Moreno Arribas 180070
 Jorge Albendea Pizarro 190229

CPU signals

Question 1 States diagram

Question 2 States decoder

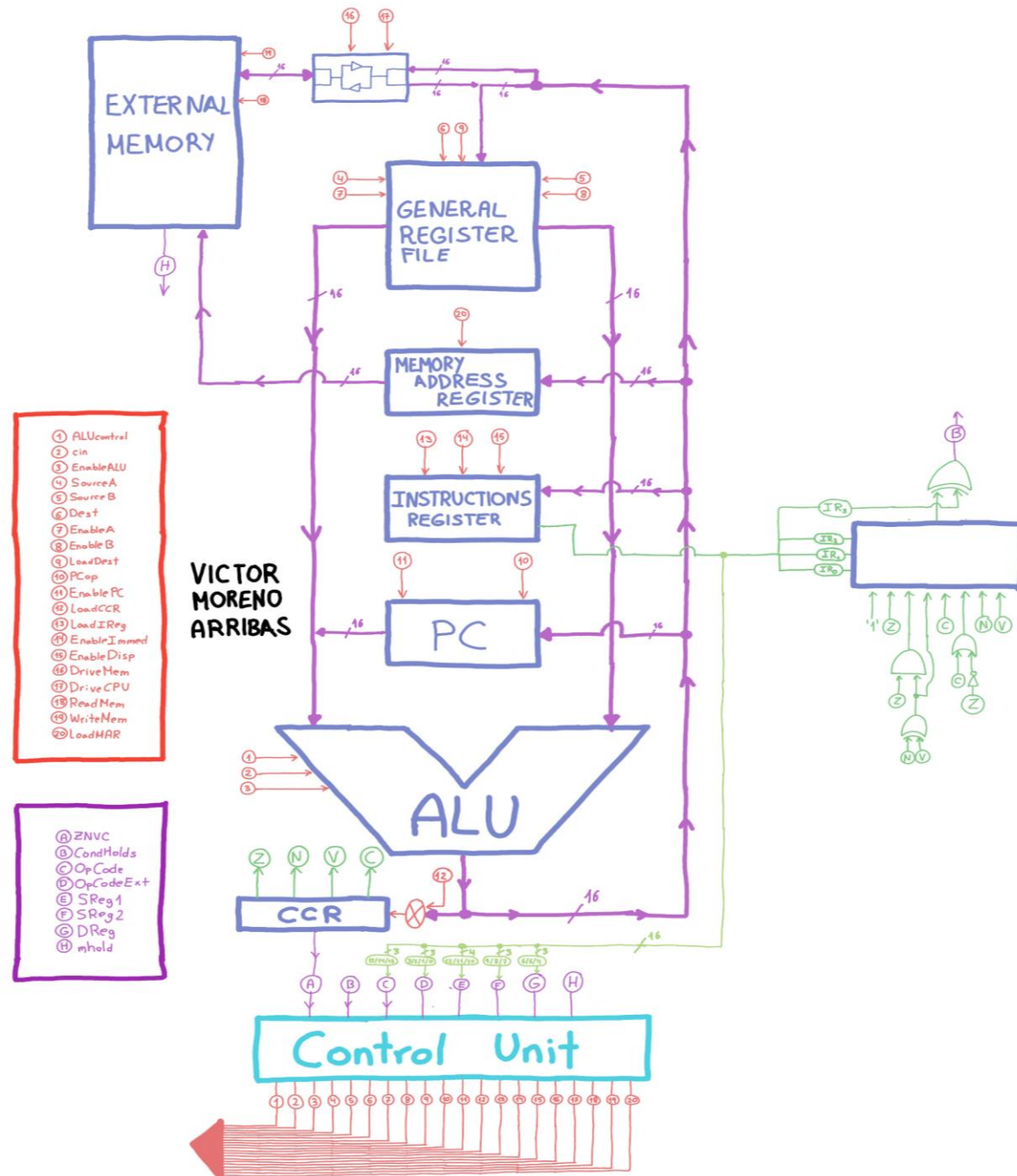


CPU signals

Question 1

States diagram

Question 2

States decoder

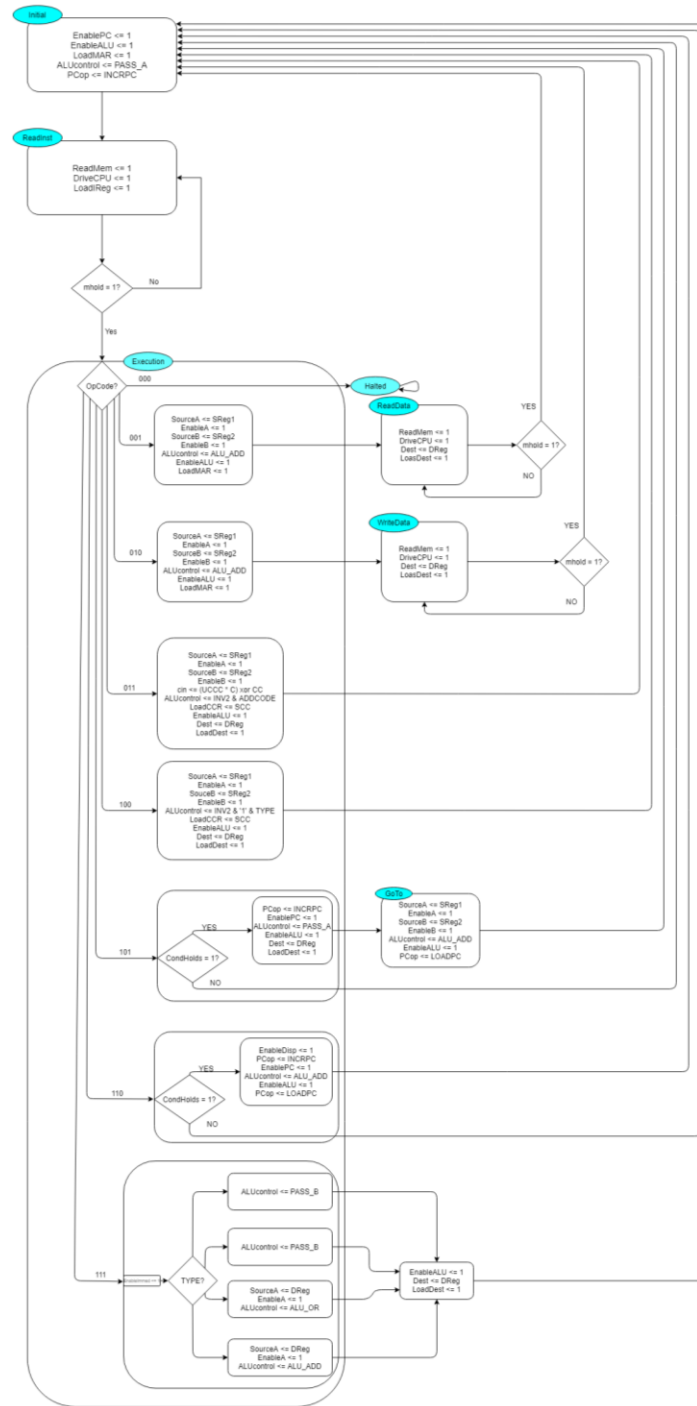

CPU signals

Question 1 States diagram


Question 2 States decoder

Truth table

A	B	C	States
0	0	0	Initial
0	0	1	ReadInst
0	1	0	Execution
0	1	1	ReadData
1	0	0	WriteData
1	0	1	GoTo
1	1	0	Halted
1	1	1	Error

Minterm Equations

Initial = $\bar{A} \cdot \bar{B} \cdot \bar{C}$
ReadInst = $\bar{A} \cdot \bar{B} \cdot C$
Execution = $\bar{A} \cdot B \cdot \bar{C}$
ReadData = $\bar{A} \cdot B \cdot C$
WriteData = $A \cdot \bar{B} \cdot \bar{C}$
GoTo = $A \cdot \bar{B} \cdot C$
Halted = $A \cdot B \cdot \bar{C}$
Error = $A \cdot B \cdot C$

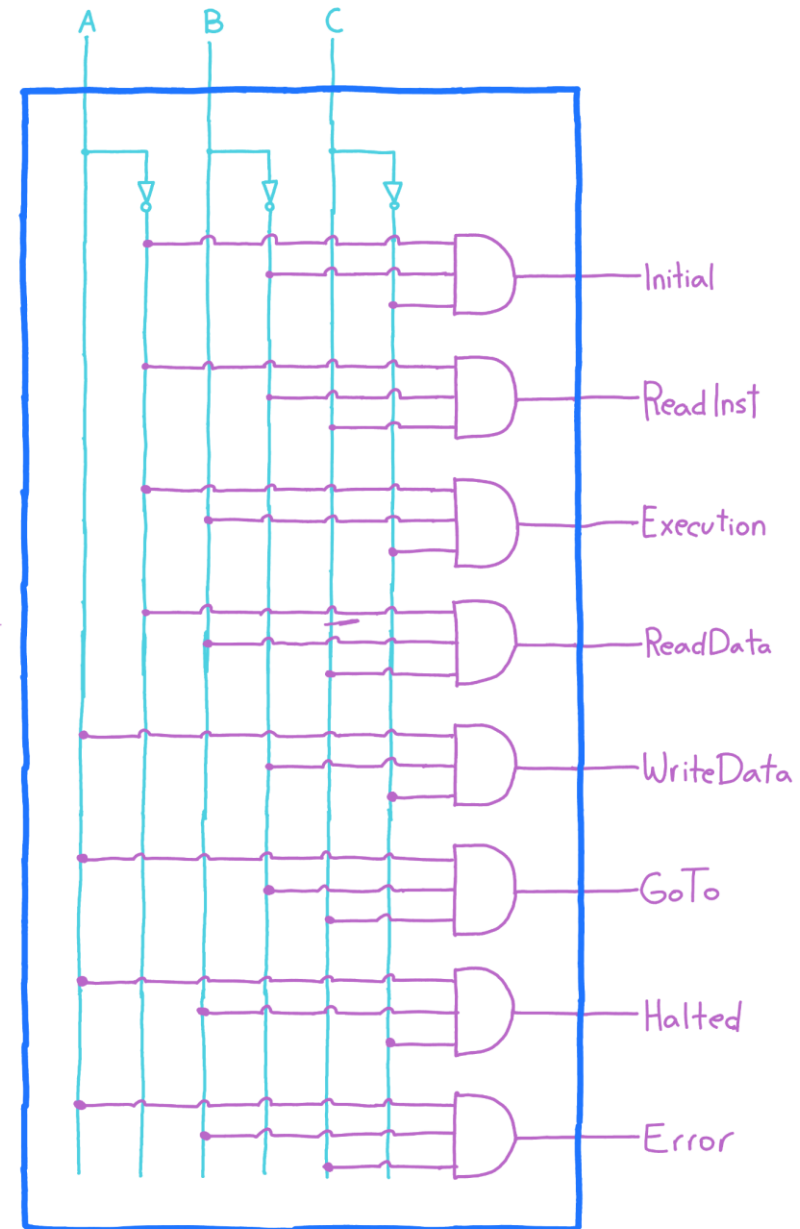

DECODER 3:8